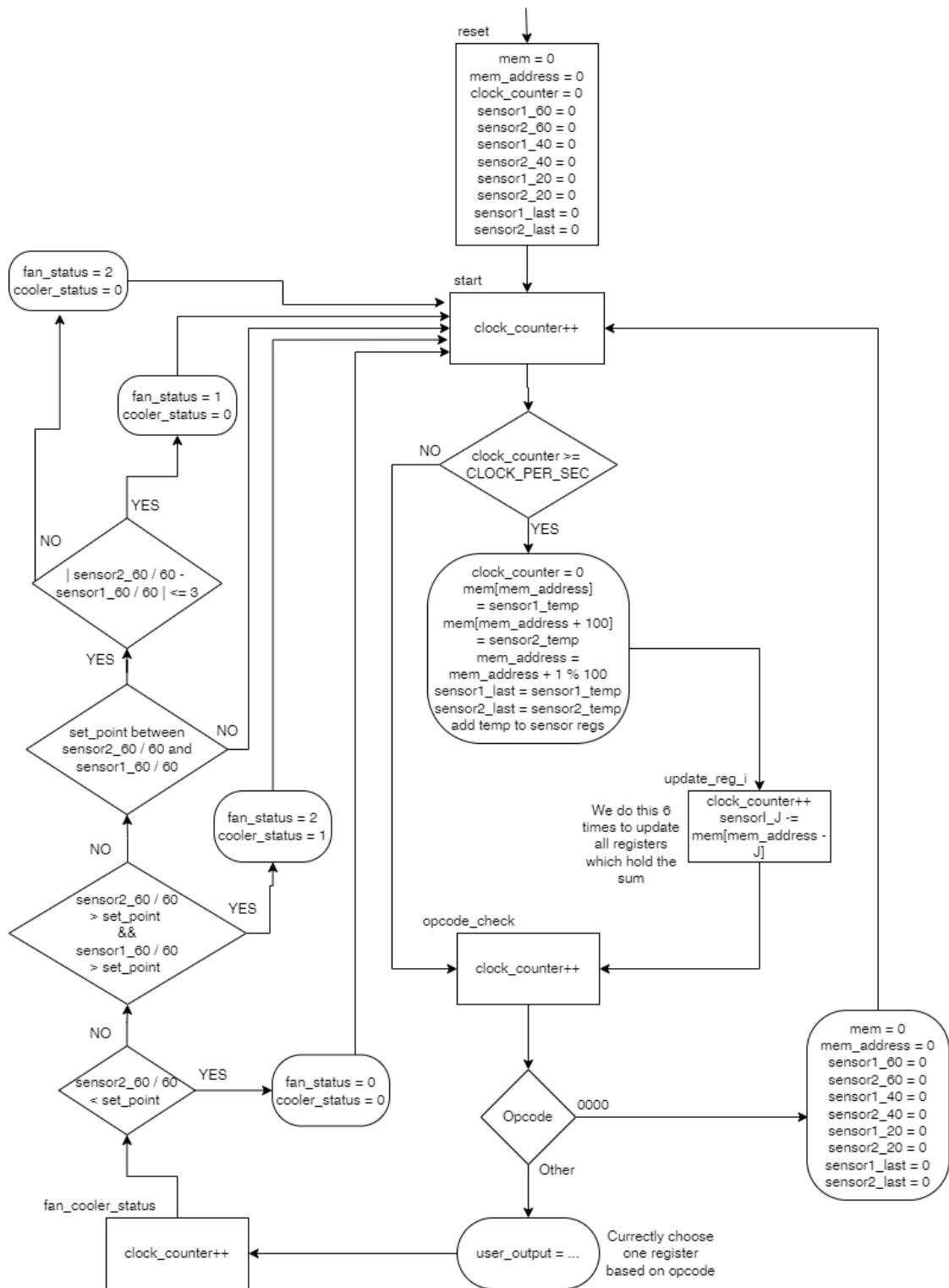



در ابتدا سعی می‌کنیم که ASM Chart مدار را طراحی کنیم. در طراحی من فرض شده است که هشت رجیستر داریم. برای هر دو سنسور چهار تا. یکی از آنها آخرین دمای ذخیره سازی شده را نگه داری می‌کنید. سه تای دیگر مجموع ۲۰، ۴۰ و ۶۰ ثانیه‌ی قبل را نگه داری می‌کنند. نکته‌ی مهمی که در این طراحی وجود دارد این است که فرض شده است در هر ثانیه مدار چندین کلاک می‌خورد. (با توجه به FSM حداقل ۱۰ کلاک). دلیل نیاز داشتن به چندین کلاک این است که مموری ما یک خط آدرس و خروجی دارد. پس در هر کلاک فقط می‌توان یک عدد از آن خواند و نوشت و ما نیاز داریم که ۶ عدد از مموری بخوانیم (دمای ۲۰، ۴۰ و ۶۰ ثانیه‌ی گذشته) که بتوانیم آنها را از رجیسترها کم کنیم. همچنین برای ذخیره سازی دمای در حال حاضر نیز به دو کلاک زمان نیاز داریم. حال مسئله‌ای که به وجود می‌آید این است که چطور می‌شود فهمید که کی یک ثانیه گذشته است. برای این موضوع از یک counter استفاده می‌کنیم. این counter در هر کلاک یکی روبه بالا می‌شمارد. در صورتی که عدد این counter از فرکانس مدار بیشتر شد، یک ثانیه گذشته است و باید که دمای جدید را خواند. دقت کنید که فرکانس مدار باید قبل از شروع مدار معلوم باشد. به همین منظور در طراحی نهایی من فرکانس را پارامتر کرده‌ام که به راحتی قابل تغییر باشد. همچنین دقت کنید که زمانی که این شمارنده بیشتر از فرکانس شد باید فرکانس را از آن کم کنیم.

من این سوال را به کمک یک مموری حل کردم. برای راحت تر شدن کار فرض کرده‌ام که ۱۰۰ خانه‌ی اول مموری برای سنسور اول هستند و ۱۰۰ خانه‌ی بعدی برای سنسور ۲. برای نگه داری آخرین آدرس نوشته شده در مموری از تنها یک شمارنده استفاده می‌کنیم که می‌تواند تا ۱۰۰ بشمارد و سپس ۰ می‌شود.

قسمت چک کردن opcode و تعیین حالت فن نیز به صورت روتین و نرمال انجام می‌شود. می‌توانید ASM Chart مدار را در صفحه‌ی بعد مشاهده کنید.



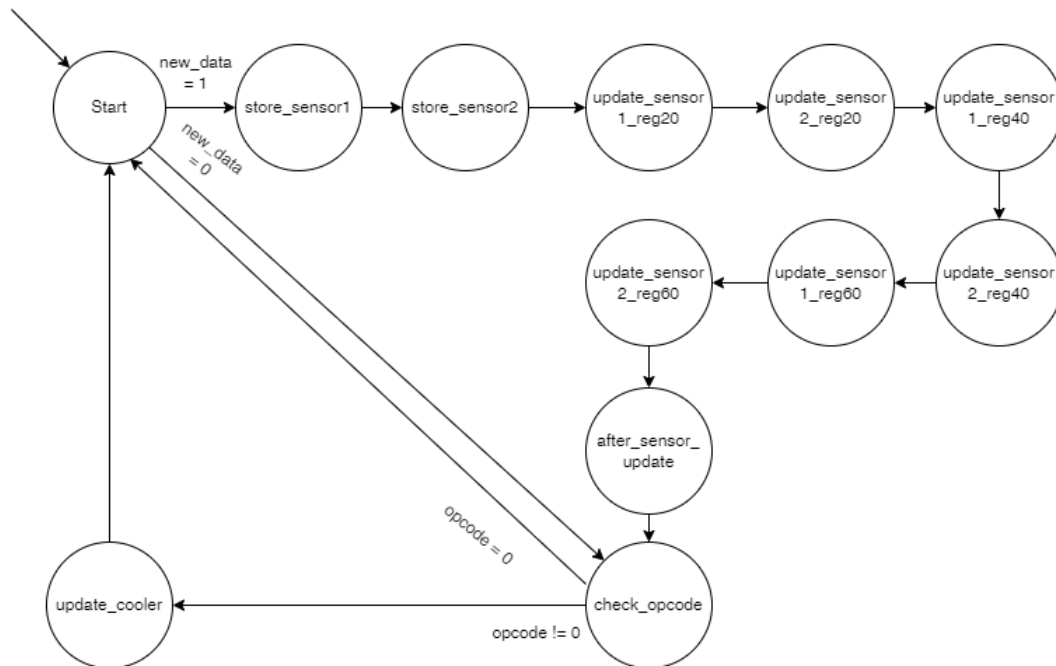حال با توجه به این ASM Chart می‌توان یک state diagram با FSM طراحی کرد.



حال ماژول‌های مورد نیاز را طراحی می‌کنیم. در ابتدا برای رجیسترهای نگه دارنده‌ی آخرین دمای هر سنسور باید از DFFهایی استفاده کنیم که قابلیت load یا enable داشته باشد.

```

1 module DFFWithLoad #(parameter WIDTH = 8) (
2     input wire clk,
3     input wire clear,
4     input wire load,
5     input wire [WIDTH-1:0] in,
6     output reg [WIDTH-1:0] out
7 );
8     always @(posedge clk or posedge clear) begin
9         if (clear)
10            out <= 0;
11        else if (load)
12            out <= in;
13    end
14 endmodule
  
```

حال برای رجیسترهای نگه دارنده‌ی جمع دما باید از رجیسترهایی استفاده کنیم که قابلیت جمع و تفریق یک عدد را نیز با عدد نگه داری شده در خودشان داشته باشند. همچنین امکان enable را به آن اضافه می‌کنیم که در صورتی که فعال نباشد عدد خروجی تغییری نمی‌کند. همچنین برای تعیین جمع یا تفریق از یک سیگنال استفاده می‌کنیم که زمانی که ۱ باشد تفریق و در غیر این صورت جمع انجام می‌شود.

```

1 module SensorSumHolder #(parameter WIDTH = 16) (
2     input wire clk,
  
```

```

3   input wire reset,
4   input wire enable, // if enable is zero nothing will be changed
5   input wire sub_sum_not, // if 0 out will be in + out otherwise out =
   out - in
6   input wire signed [WIDTH-1:0] in,
7   output reg signed [WIDTH-1:0] out
8 );
9   always @(posedge clk or posedge reset) begin
10      if (reset)
11         out <= 0;
12      else if (enable) begin
13         if (sub_sum_not) begin
14            out <= out - in;
15         end else begin
16            out <= out + in;
17         end
18      end
19   end
20 endmodule

```

برای شمارنده‌ی کلاک و آدرس مموری یک شمارنده طراحی می‌کنیم که عددی به عنوان باقی‌مانده می‌گیرد و در زمان شمارش، عدد را بر پیمانه‌ی آن عدد حساب می‌کند. همچنین برای این این شمارنده یک سیگنال enable قرار می‌دهیم که مشخص می‌کند که آیا باید روبه بالا بشمارد یا عدد قبلی را خروجی دهد. همچنین یک سیگنال mod enable برای آن قرار می‌دهیم که مشخص می‌کند که آیا باید زمان شمردن بالا باقی مانده نیز بگیرد یا خیر. کد این قطعه به صورت زیر است.

```

1 module CounterWithMod #(parameter WIDTH = 8, parameter MOD = 100) (
2   input wire clk,
3   input wire clear,
4   input wire enable,
5   input wire mod_enable,
6   output reg [WIDTH-1:0] out
7 );
8   always @(posedge clk or posedge clear) begin
9      if (clear)
10         out <= 0;
11      else if (enable) begin
12         if (mod_enable)
13            out <= (out + 1) % MOD;
14         else
15            out <= out + 1;
16      end
17   end
18 endmodule

```

حال برای خروجی دادن با توجه به opcode ورودی کاربر نیاز به یک mux ۸ به ۱ داریم. کد این مالتیپلکسر در زیر آمده است:

```

1 module Mux8To1 #(parameter WIDTH = 8) (
2   input wire [WIDTH-1:0] a,
3   input wire [WIDTH-1:0] b,

```

```

4     input wire [WIDTH-1:0] c,
5     input wire [WIDTH-1:0] d,
6     input wire [WIDTH-1:0] e,
7     input wire [WIDTH-1:0] f,
8     input wire [WIDTH-1:0] g,
9     input wire [WIDTH-1:0] h,
10    input wire [2:0] select,
11    output reg [WIDTH-1:0] out
12);
13    always @(*) begin
14        case(select)
15            3'b000: out = a;
16            3'b001: out = b;
17            3'b010: out = c;
18            3'b011: out = d;
19            3'b100: out = e;
20            3'b101: out = f;
21            3'b110: out = g;
22            3'b111: out = h;
23        endcase
24    end
25endmodule

```

در نهایت باید ماژولی طراحی کنیم که با توجه به دمای یک دقیقه‌ای اخیر و set point وضعیت فن و خنک کننده را مشخص کنید. در ابتدا برای تشخیص وضعیت به یک قدر مطلق گیر و تشخیص دهمی بودن در یک بازه نیاز داریم. ماژول قدر مطلق گیر به صورت زیر است:

```

1 module Abs #(parameter WIDTH = 8) (
2     input wire [WIDTH-1:0] in,
3     output wire [WIDTH-1:0] out
4 );
5     assign out = in[WIDTH-1] ? -in : in;
6 endmodule

```

حال ماژولی طراحی می‌کنیم که مشخص کنید که آیا عددی بین دو عدد دیگر است یا خیر. برای این کار ابتدا boundry بازه را سورت می‌کنیم و با دو مقایسه جواب را بدست می‌آوریم. دقت کنید که برای اینکه مقایسه در اعداد صحیح درست انجام بگیرد تمامی سیم‌ها را signed تعریف می‌کنیم.

```

1 module BetweenChecker #(parameter WIDTH = 8) (
2     input wire signed [WIDTH-1:0] a,
3     input wire signed [WIDTH-1:0] b,
4     input wire signed [WIDTH-1:0] target,
5     output wire result
6 );
7     wire signed [WIDTH-1:0] lower = a > b ? b : a;
8     wire signed [WIDTH-1:0] upper = a > b ? a : b;
9     assign result = target > lower & target < upper;
10 endmodule

```

حال ماژول مشخص کننده وضعیت خنک کننده و فن را طراحی می‌کنیم.

```

1 `include "Abs.v"
2 `include "BetweenChecker.v"
3
4 module FanStatusResultFinder (
5     input wire signed [7:0] sensor1_60_average,
6     input wire signed [7:0] sensor2_60_average,
7     input wire signed [7:0] set_point,
8     output reg [1:0] result
9 );
10 // Get the abs of difference
11 wire [7:0] abs_diff;
12 Abs #(8) abs(sensor2_60_average - sensor1_60_average, abs_diff);
13
14 // Check if set point is in between
15 wire set_point_between_averages;
16 BetweenChecker #(8) between_checker(sensor1_60_average,
17 sensor2_60_average, set_point, set_point_between_averages);
18
19 always @(*) begin
20     if (sensor2_60_average < set_point)
21         result = 0;
22     else if (sensor2_60_average > set_point & sensor1_60_average >
23 set_point)
24         result = 1;
25     else if (set_point_between_averages) begin
26         if (abs_diff <= 3)
27             result = 2;
28         else
29             result = 3;
30     end
31 end
32 endmodule

```

در نهایت به کمک این قطعات کل datapath را طراحی می‌کنیم. ورودی و خروجی‌های آن به صورت زیر هستند:

- `reset_clock_counter`: مود باقی مانده‌گیر شمارنده‌ی کلاک را فعال می‌کند.
- `reset_sum_registers`: رجیسترهایی که جمع را نگه داری می‌کند را صفر می‌کند. در زمانی استفاده می‌شود که آپکد برابر ۰ باشد.
- `new_temp_ready`: زمانی یک می‌شود که نیاز به گرفتن ورودی دمای جدید هستیم.
- `sensor1_in`: دمایی که باید با رجیسترهای سنسور یک جمع یا تفریق شود.
- `sensor2_in`: دمایی که باید با رجیسترهای سنسور دو جمع یا تفریق شود.
- `sensor1_last_load`: مشخص می‌کند که آیا باید ورودی در رجیستر آخرین دمای سنسور اول ذخیره شود یا خیر.
- `sensor2_last_load`: مشخص می‌کند که آیا باید ورودی در رجیستر آخرین دمای سنسور دوم ذخیره شود یا خیر.

- سیگنال‌های کنترلی مربوط به میانگین: برای هر سنسور سه SensorSumHolder استفاده کردم. هر کدام از این سنسورها دو ورودی دارند که باید توسط CU مشخص شوند. یکی فعال بودن آنها هست و یکی مود بین تفریق و جمع. هر سنسور سه رجیستر دارد پس یک آرایه‌ی بیتی به طول ۳ برای هر سنسور در نظر گرفته شده است.
- average_select: عدد داده شده نشان می‌دهد که کدام یک از رجیسترهای مربوط به میانگین دما باید در average_output ظاهر شود.
- memory_address_count_up: در صورتی که سیگنال یک باشد شمارنده آدرس مموری یکی زیاد می‌شود.
- memory_select: در صورتی که یک باشد به محلی از حافظه دسترسی پیدا می‌کنیم که برای سنسور دو است. در غیر این صورت برای سنسور یک انتخاب می‌شود.
- set_point: مستقیم از خود قطعه می‌آید.
- fan_status_result: حالت‌های خروجی در زیر آمده است:

۱. فن و خنک کننده خاموش

۲. فن دور تند و خنک کننده روشن

۳. فن روشن با دور کم خنک کننده خاموش

۴. فن روشن با دور تند خنک کننده خاموش

```

1 `include "CounterWithMod.v"
2 `include "dff_load.v"
3 `include "SensorSumHolder.v"
4 `include "Mux8To1.v"
5 `include "FanStatusFinder.v"
6
7 module Datapath #(parameter CLOCK_FREQUENCY = 10000) (
8     input wire clk,
9     input wire reset,
10    input wire reset_clock_counter,
11    input wire reset_sum_registers,
12    output wire new_temp_ready,
13    // Sum saver registers
14    input wire [7:0] sensor1_in,
15    input wire [7:0] sensor2_in,
16    input wire sensor1_last_load,
17    input wire sensor2_last_load,
18    // Each bit of these inputs will enable one of the chips (so several
19    chips can be enabled together)
20    input wire [2:0] sensor1_average_enable,
21    input wire [2:0] sensor2_average_enable,
22    input wire [2:0] sensor1_average_mode,
23    input wire [2:0] sensor2_average_mode,
24    // We need the raw output of these
25    input wire [2:0] average_select,
26    output wire signed [7:0] average_output,
27    // Memory stuff

```

```

27     input wire memory_address_count_up,
28     input wire memory_select,
29     input wire [1:0] memory_old_select, // 0: 0 / 1: -20 / 2: -40 / 3:
-60
30     output wire [7:0] memory_address,
31     // Fan controller stuff
32     input wire signed [7:0] set_point,
33     output wire [1:0] fan_status_result
34 );
35 // Sign extend inputs
36 wire [15:0] sensor1_in_sign_extend = {{8{sensor1_in[7]}}}, sensor1_in
[7:0]};
37 wire [15:0] sensor2_in_sign_extend = {{8{sensor2_in[7]}}}, sensor2_in
[7:0]};
38
39 // Sum saver registers
40 wire signed [7:0] sensor1_last_out, sensor2_last_out;
41 DFFWithLoad #(.WIDTH(8)) sensor1_last(clk, reset |
reset_sum_registers, sensor1_last_load, sensor1_in, sensor1_last_out
);
42 DFFWithLoad #(.WIDTH(8)) sensor2_last(clk, reset |
reset_sum_registers, sensor2_last_load, sensor2_in, sensor2_last_out
);
43 wire signed [15:0] sensor1_20_out, sensor2_20_out, sensor1_40_out,
sensor2_40_out, sensor1_60_out, sensor2_60_out;
44 SensorSumHolder #(.WIDTH(16)) sensor1_20(.clk(clk), .reset(reset |
reset_sum_registers), .enable(sensor1_average_enable[0]), .
sub_sum_not(sensor1_average_mode[0]), .in(sensor1_in_sign_extend), .
out(sensor1_20_out));
45 SensorSumHolder #(.WIDTH(16)) sensor2_20(.clk(clk), .reset(reset |
reset_sum_registers), .enable(sensor2_average_enable[0]), .
sub_sum_not(sensor2_average_mode[0]), .in(sensor2_in_sign_extend), .
out(sensor2_20_out));
46 SensorSumHolder #(.WIDTH(16)) sensor1_40(.clk(clk), .reset(reset |
reset_sum_registers), .enable(sensor1_average_enable[1]), .
sub_sum_not(sensor1_average_mode[1]), .in(sensor1_in_sign_extend), .
out(sensor1_40_out));
47 SensorSumHolder #(.WIDTH(16)) sensor2_40(.clk(clk), .reset(reset |
reset_sum_registers), .enable(sensor2_average_enable[1]), .
sub_sum_not(sensor2_average_mode[1]), .in(sensor2_in_sign_extend), .
out(sensor2_40_out));
48 SensorSumHolder #(.WIDTH(16)) sensor1_60(.clk(clk), .reset(reset |
reset_sum_registers), .enable(sensor1_average_enable[2]), .
sub_sum_not(sensor1_average_mode[2]), .in(sensor1_in_sign_extend), .
out(sensor1_60_out));
49 SensorSumHolder #(.WIDTH(16)) sensor2_60(.clk(clk), .reset(reset |
reset_sum_registers), .enable(sensor2_average_enable[2]), .
sub_sum_not(sensor2_average_mode[2]), .in(sensor2_in_sign_extend), .

```



```

out(sensor2_60_out));

50
51 // Averages
52 wire signed [7:0] sensor1_20_average = sensor1_20_out / 20;
53 wire signed [7:0] sensor2_20_average = sensor2_20_out / 20;
54 wire signed [7:0] sensor1_40_average = sensor1_40_out / 40;
55 wire signed [7:0] sensor2_40_average = sensor2_40_out / 40;
56 wire signed [7:0] sensor1_60_average = sensor1_60_out / 60;
57 wire signed [7:0] sensor2_60_average = sensor2_60_out / 60;
58 Mux8To1 average_result_mux(
59     .a(sensor1_last_out),
60     .b(sensor2_last_out),
61     .c(sensor1_20_average),
62     .d(sensor2_20_average),
63     .e(sensor1_40_average),
64     .f(sensor2_40_average),
65     .g(sensor1_60_average),
66     .h(sensor2_60_average),
67     .select(average_select),
68     .out(average_output)
69 );
70
71 // Clock counter
72 wire [31:0] clock_counter;
73 CounterWithMod #(.WIDTH(32), .MOD(CLOCK_FREQUENCY))
74 clock_counter_part(.clk(clk), .clear(reset), .enable(1'b1), .
75 mod_enable(reset_clock_counter), .out(clock_counter));
76 assign new_temp_ready = clock_counter >= CLOCK_FREQUENCY;
77
78 // Mem address
79 wire [7:0] mem_address;
80 CounterWithMod #(.WIDTH(8), .MOD(100)) mem_address_counter(.clk(clk)
81 , .clear(reset), .enable(memory_address_count_up), .mod_enable(1'b1)
82 , .out(mem_address));
83 wire [31:0] offset_memory_address = (mem_address + memory_old_select
84 * 80) % 100;
85 assign memory_address = memory_select ? offset_memory_address + 100
86 : offset_memory_address;
87
88 // Fan result
89 FanStatusResultFinder fan_result_finder(.sensor1_60_average(
90 sensor1_60_average), .sensor2_60_average(sensor2_60_average), .
91 set_point(set_point), .result(fan_status_result));
92 endmodule

```

حال با توجه به نمودار حالت control unit را طراحی می‌کنیم. سعی کرده‌ام که با کامنت توضیحاتی درباره‌ی قسمت‌های مختلف بدهم.

```

1 module ControlUnit(

```

```

2   input wire clk,
3   input wire reset,
4   //////////////////////////////////////////////////
5   // Main Controller //
6   //////////////////////////////////////////////////
7   input wire [3:0] microupcode,
8   input wire signed [7:0] sensor1_temp,
9   input wire signed [7:0] sensor2_temp,
10  output reg [1:0] fan_status,
11  output reg cooler_status,
12  //////////////////////////////////////////////////
13  // Datapath //
14  //////////////////////////////////////////////////
15  output reg reset_clock_counter,
16  output reg reset_sum_registers,
17  input wire new_temp_ready,
18  // Sum saver registers
19  output reg [7:0] sensor1_in,
20  output reg [7:0] sensor2_in,
21  output reg sensor1_last_load,
22  output reg sensor2_last_load,
23  // Each bit of these inputs will enable one of the chips (so several
  chips can be enabled together)
24  output reg [2:0] sensor1_average_enable,
25  output reg [2:0] sensor2_average_enable,
26  output reg [2:0] sensor1_average_mode,
27  output reg [2:0] sensor2_average_mode,
28  // We need the raw output of these
29  output reg [2:0] average_select,
30  // Memory stuff
31  output reg datapath_memory_address_count_up,
32  output reg datapath_memory_select,
33  output reg [1:0] memory_old_select,
34  // Fan controller stuff
35  input wire [1:0] fan_status_result,
36  //////////////////////////////////////////////////
37  // RAM //
38  //////////////////////////////////////////////////
39  output reg ram_write_enable,
40  inout [7:0] ram_inout,
41  output reg ram_reset
42 );
43 // State stuff
44 localparam [3:0] STATE_START = 0, STATE_STORE_SENSOR1 = 1,
  STATE_STORE_SENSOR2 = 2,
45     STATE_UPDATE_SENSOR1_REG20 = 3, STATE_UPDATE_SENSOR2_REG20 = 4,
46     STATE_UPDATE_SENSOR1_REG40 = 5, STATE_UPDATE_SENSOR2_REG40 = 6,
47     STATE_UPDATE_SENSOR1_REG60 = 7, STATE_UPDATE_SENSOR2_REG60 = 8,

```

```

48     STATE_CHECK_UPCODE = 9, STATE_UPDATE_COOLER = 10,
STATE_AFTER_SENSOR_UPDATE = 11;
49     reg [3:0] state, next_state;
50
51     // Ram
52     reg [7:0] ram_output;
53     assign ram_inout = ram_write_enable ? ram_output : 8'bz;
54
55     // Combinational part
56     always @(*) begin
57         // Reset status registers
58         reset_clock_counter = 0;
59         reset_sum_registers = 0;
60         ram_write_enable = 0;
61         ram_reset = 0;
62         sensor1_last_load = 0;
63         sensor2_last_load = 0;
64         sensor1_average_enable = 0;
65         sensor2_average_enable = 0;
66         datapath_memory_address_count_up = 0;
67         // Check state
68         case(state)
69             STATE_START: begin
70                 if (new_temp_ready) begin
71                     next_state = STATE_STORE_SENSOR1;
72                     reset_clock_counter = 1;
73                 end else begin
74                     next_state = STATE_CHECK_UPCODE;
75                 end
76             end
77             STATE_STORE_SENSOR1: begin
78                 datapath_memory_select = 0; // first sensor
79                 memory_old_select = 0; // current index
80                 ram_output = sensor1_temp; // save temp 1
81                 sensor1_in = sensor1_temp;
82                 ram_write_enable = 1; // write to ram
83                 sensor1_last_load = 1;
84                 sensor1_average_enable = 3'b111; // add to all
85                 sensor1_average_mode = 3'b000; // mode add
86                 next_state = STATE_STORE_SENSOR2;
87             end
88             STATE_STORE_SENSOR2: begin
89                 datapath_memory_select = 1; // second sensor
90                 memory_old_select = 0; // current index
91                 ram_output = sensor2_temp; // save temp 2
92                 sensor2_in = sensor2_temp;
93                 ram_write_enable = 1; // write to ram
94                 sensor2_last_load = 1;

```

```

95         sensor2_average_enable = 3'b111; // add to all
96         sensor2_average_mode = 3'b000; // mode add
97         next_state = STATE_UPDATE_SENSOR1_REG20;
98     end
99     STATE_UPDATE_SENSOR1_REG20: begin
100         datapath_memory_select = 0; // first sensor
101         memory_old_select = 1; // -20
102         // We edit the reg in next state
103         next_state = STATE_UPDATE_SENSOR2_REG20;
104     end
105     STATE_UPDATE_SENSOR2_REG20: begin
106         // Update the sensor from previous state
107         sensor1_average_enable = 3'b001; // sub from first
108         sensor1_average_mode = 3'b001; // mode sub
109         sensor1_in = ram_inout;
110         // Update ram
111         datapath_memory_select = 1; // second sensor
112         memory_old_select = 1; // -20
113         next_state = STATE_UPDATE_SENSOR1_REG40;
114     end
115     STATE_UPDATE_SENSOR1_REG40: begin
116         // Update the sensor
117         sensor2_average_enable = 3'b001; // sub from first
118         sensor2_average_mode = 3'b001; // mode sub
119         sensor2_in = ram_inout;
120         // Update ram
121         datapath_memory_select = 0; // first sensor
122         memory_old_select = 2; // -40
123         next_state = STATE_UPDATE_SENSOR2_REG40;
124     end
125     STATE_UPDATE_SENSOR2_REG40: begin
126         // Update the sensor
127         sensor1_average_enable = 3'b010;
128         sensor1_average_mode = 3'b010; // mode sub
129         sensor1_in = ram_inout;
130         // Update ram
131         datapath_memory_select = 1; // second sensor
132         memory_old_select = 2; // -40
133         next_state = STATE_UPDATE_SENSOR1_REG60;
134     end
135     STATE_UPDATE_SENSOR1_REG60: begin
136         // Update the sensor
137         sensor2_average_enable = 3'b010;
138         sensor2_average_mode = 3'b010; // mode sub
139         sensor2_in = ram_inout;
140         // Update ram
141         datapath_memory_select = 0; // first sensor
142         memory_old_select = 3; // -60

```

```

143         next_state = STATE_UPDATE_SENSOR2_REG60;
144     end
145     STATE_UPDATE_SENSOR2_REG60: begin
146         // Update the sensor
147         sensor1_average_enable = 3'b100;
148         sensor1_average_mode = 3'b100; // mode sub
149         sensor1_in = ram_inout;
150         // Update ram
151         datapath_memory_select = 1; // second sensor
152         memory_old_select = 3; // -60
153         next_state = STATE_AFTER_SENSOR_UPDATE;
154     end
155     STATE_AFTER_SENSOR_UPDATE: begin
156         // Update the sensor
157         sensor2_average_enable = 3'b100;
158         sensor2_average_mode = 3'b100; // mode sub
159         sensor2_in = ram_inout;
160         datapath_memory_address_count_up = 1; // increase memory
address
161         // Done
162         next_state = STATE_CHECK_UPCODE;
163     end
164     STATE_CHECK_UPCODE: begin
165         case (microupcode)
166             4'b0000: begin
167                 reset_sum_registers = 1;
168                 ram_reset = 1;
169             end
170             4'b1000: average_select = 0;
171             4'b1100: average_select = 1;
172             4'b1001: average_select = 2;
173             4'b1010: average_select = 4;
174             4'b1011: average_select = 6;
175             4'b1101: average_select = 3;
176             4'b1110: average_select = 5;
177             4'b1111: average_select = 7;
178         endcase
179         next_state = microupcode == 0 ? STATE_START :
STATE_UPDATE_COOLER;
180     end
181     STATE_UPDATE_COOLER: begin
182         // This is combinational so we can do this
183         case (fan_status_result)
184             2'b00: begin
185                 fan_status = 0;
186                 cooler_status = 0;
187             end
188             2'b01: begin

```

```

189         fan_status = 2;
190         cooler_status = 1;
191     end
192     2'b10: begin
193         fan_status = 1;
194         cooler_status = 0;
195     end
196     2'b11: begin
197         fan_status = 2;
198         cooler_status = 0;
199     end
200     endcase
201     next_state = STATE_START;
202 end
203 endcase
204 end
205
206 // Sequential part
207 always @(posedge clk or posedge reset) begin
208     if (reset)
209         state <= STATE_START;
210     else
211         state <= next_state;
212 end
213 endmodule

```

حال مموری را طراحی می‌کنیم:

```

1 module Memory (
2     input wire clk,
3     input wire reset,
4     input wire [7:0] addr, // 8 bit address to access at last 256
5     input wire write_enable,
6     inout [7:0] data
7 );
8     reg [7:0] mem[0:199];
9     reg [7:0] read_data;
10    integer i;
11
12    assign data = write_enable ? 8'bz : read_data;
13
14    always @(posedge clk or posedge reset) begin
15        if (reset)
16            for (i = 0; i < 200; i = i + 1)
17                mem[i] <= 0;
18        else if (write_enable)
19            mem[addr] <= data;
20        else
21            read_data <= mem[addr];

```

```

22     end
23 endmodule

```

در نهایت نیز تمامی قطعات را به هم می‌چسبانیم.

```

1  `include "Memory.v"
2  `include "Datapath.v"
3  `include "ControlUnit.v"
4
5  module FanController #(parameter CLOCK_FREQUENCY = 10000) (
6      input wire clk,
7      input wire reset,
8      input wire [3:0] microupcode,
9      input wire signed [7:0] set_point,
10     input wire signed [7:0] sensor1_temp,
11     input wire signed [7:0] sensor2_temp,
12     output wire [1:0] fan_status,
13     output wire cooler_status,
14     output wire [7:0] user_output
15 );
16     wire [7:0] mem_address, mem_inout;
17     wire mem_wire_enable, mem_reset;
18     Memory ram (.clk(clk), .reset(reset | mem_reset), .addr(mem_address)
19     , .write_enable(mem_wire_enable), .data(mem_inout));
20
21     wire reset_clock_counter, reset_sum_registers, new_temp_ready,
22     sensor1_last_load, sensor2_last_load, memory_address_count_up,
23     memory_select;
24     wire [7:0] sensor1_in, sensor2_in;
25     wire [2:0] sensor1_average_enable, sensor2_average_enable,
26     sensor1_average_mode, sensor2_average_mode, average_select;
27     wire [1:0] fan_status_result, memory_old_select;
28     Datapath #(CLOCK_FREQUENCY) datapath(
29         .clk(clk),
30         .reset(reset),
31         .reset_clock_counter(reset_clock_counter),
32         .reset_sum_registers(reset_sum_registers),
33         .new_temp_ready(new_temp_ready),
34         .sensor1_in(sensor1_in),
35         .sensor2_in(sensor2_in),
36         .sensor1_last_load(sensor1_last_load),
37         .sensor2_last_load(sensor2_last_load),
38         .sensor1_average_enable(sensor1_average_enable),
39         .sensor2_average_enable(sensor2_average_enable),
40         .sensor1_average_mode(sensor1_average_mode),
41         .sensor2_average_mode(sensor2_average_mode),
42         .average_select(average_select),
43         .average_output(user_output),
44         .memory_address_count_up(memory_address_count_up),

```

```

41     .memory_select(memory_select),
42     .memory_old_select(memory_old_select),
43     .memory_address(mem_address),
44     .set_point(set_point),
45     .fan_status_result(fan_status_result)
46 );
47 ControlUnit cu(
48     .clk(clk),
49     .reset(reset),
50     .microupcode(microupcode),
51     .sensor1_temp(sensor1_temp),
52     .sensor2_temp(sensor2_temp),
53     .fan_status(fan_status),
54     .cooler_status(cooler_status),
55     .reset_clock_counter(reset_clock_counter),
56     .reset_sum_registers(reset_sum_registers),
57     .new_temp_ready(new_temp_ready),
58     .sensor1_in(sensor1_in),
59     .sensor2_in(sensor2_in),
60     .sensor1_last_load(sensor1_last_load),
61     .sensor2_last_load(sensor2_last_load),
62     .sensor1_average_enable(sensor1_average_enable),
63     .sensor2_average_enable(sensor2_average_enable),
64     .sensor1_average_mode(sensor1_average_mode),
65     .sensor2_average_mode(sensor2_average_mode),
66     .average_select(average_select),
67     .datapath_memory_address_count_up(memory_address_count_up),
68     .datapath_memory_select(memory_select),
69     .memory_old_select(memory_old_select),
70     .fan_status_result(fan_status_result),
71     .ram_write_enable(mem_wire_enable),
72     .ram_inout(mem_inout),
73     .ram_reset(mem_reset)
74 );
75 endmodule

```

تست مدار

حال مدار را تست می‌کنیم. برای تست دمای ورودی را ثابت نگه می‌داریم و صبر می‌کنیم که یک دقیقه از کار مدار بگذرد. سپس خروجی مدار را بررسی می‌کنیم. تمامی رجیسترها باید مقدار دماها را داشته باشند و فن به درستی تنظیم شده باشد. کد تست در زیر آمده است:

```

1 `include "FanController.v"
2
3 module FanControllerTest;
4     reg clk, reset;
5     reg [3:0] microupcode;
6     reg signed [7:0] set_point, sensor1_temp, sensor2_temp;
7     wire signed [7:0] user_output;
8     wire [1:0] fan_status;

```





```

9      wire cooler_status;
10
11      initial clk = 0;
12      always #5 clk = ~clk;
13
14      FanController #(100) fn(clk, reset, microupcode, set_point,
15      sensor1_temp, sensor2_temp, fan_status, cooler_status, user_output);
16
17      initial begin
18          microupcode = 4'b1000;
19          reset = 1;
20          #8;
21          reset = 0;
22          sensor1_temp = 100;
23          sensor2_temp = 50;
24          set_point = 10;
25          #(100 * 11 * 80);
26          $display("user output: %d fan status: %d cooler status: %d",
27          user_output, fan_status, cooler_status);
28          $finish;
29      end
30  endmodule

```

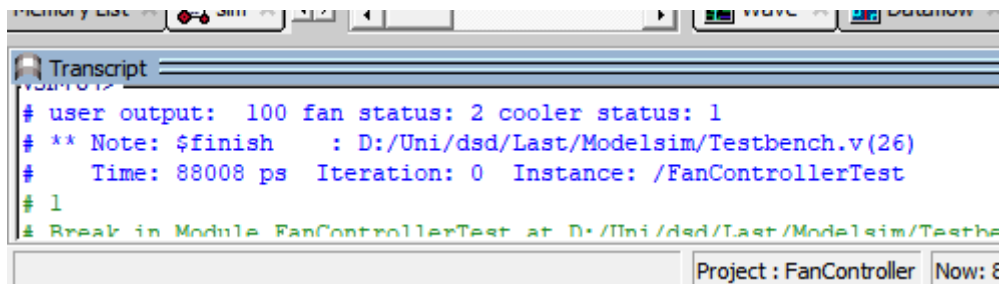بعد از تست لاگ‌های modelsim را بررسی می‌کنیم که آیا جواب درست به ما داده شده است یا خیر.



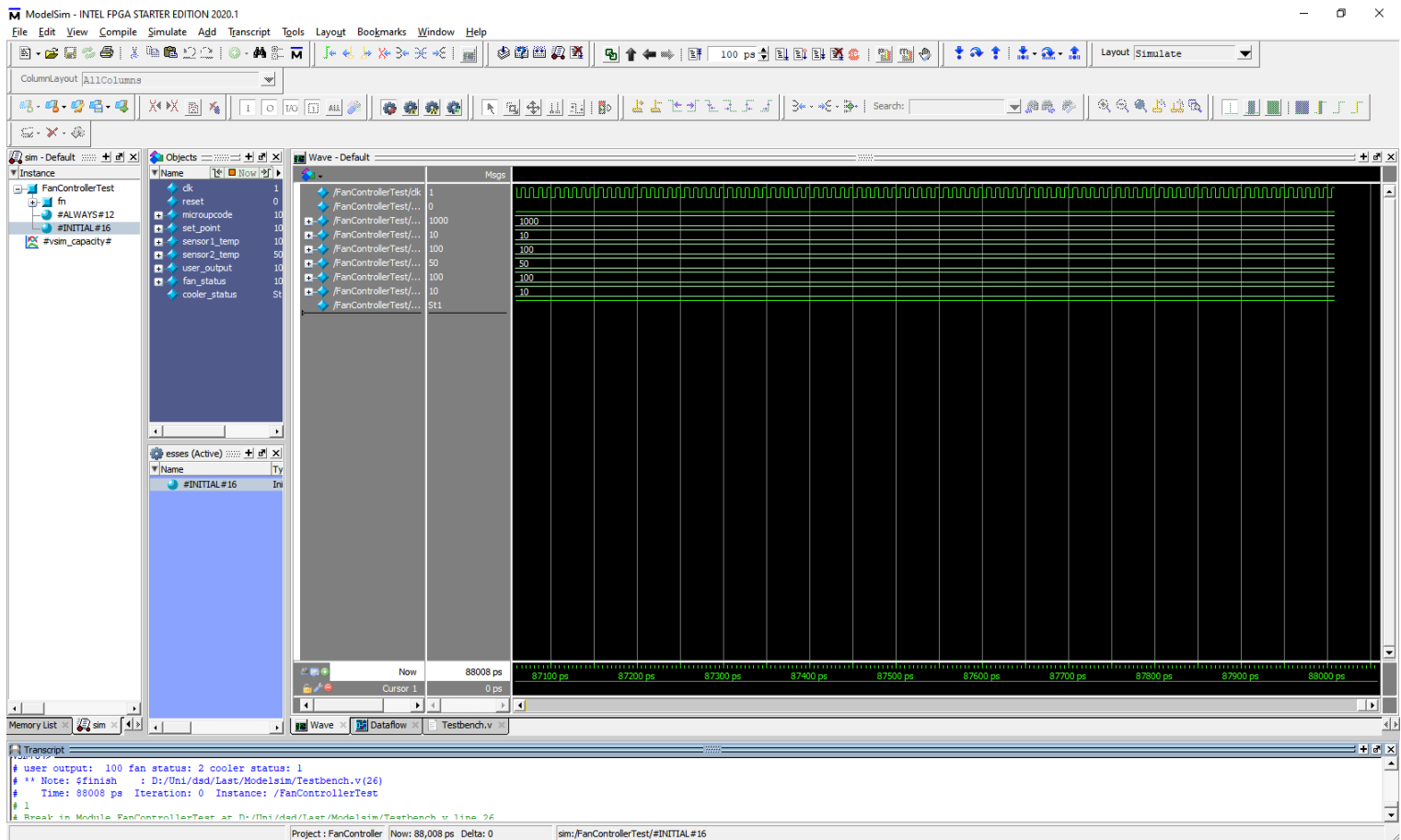

سنتز
 من سنتز را به کمک نرم افزار Quartus انجام دادم. نکته‌ای که قبل از سنتز باید توجه کرد این است که باید تمامی خط‌های include را از اول تمامی فایل‌ها برداشت چرا که کوآرتوس ارور می‌دهد. بعد از این کار، سنتز را انجام می‌دهیم و مشاهده می‌شود که به درستی سنتز انجام می‌شود. حتی می‌توان کلاک پیشنهادی مدار را نیز پیدا کرد.

Quartus Prime Lite Edition - D:/Uni/dsd/Last/Quartus/FanController - FanController

File Edit View Project Assignments Processing Tools Window Help

Search Intel FPGA

Project Navigator | Files

Files

- SensorSumHolder.v
- Mux8To1.v
- Memory.v
- FanStatusFinder.v
- FanController.v
- Divider.v
- dff_load.v
- dff.v
- Datapath.v
- CounterWithMod.v
- ControlUnit.v

Tasks

Compilation

Task

- Compile Design
- Analysis & Synthesis
- Fitter (Place & Route)
- Assembler (Generate programming)
- Timing Analysis
- EDA Netlist Writer
- Edit Settings
- Program Device (Open Programmer)

Table of Contents

- Flow Summary
- Flow Settings
- Flow Non-Default Global Settings
- Flow Elapsed Time
- Flow OS Summary
- Flow Log
- Analysis & Synthesis
- Fitter
- Flow Messages
- Flow Suppressed Messages
- Assembler
- Timing Analyzer

Flow Summary

<<Filter>>

Flow Status: Successful - Fri Jun 24 16:24:32 2022

Quartus Prime Version: 21.1.0 Build 842 10/21/2021 SJ Lite Edition

Revision Name: FanController

Top-level Entity Name: FanController

Family: Cyclone V

Device: SCGXFC7C7F23C8

Timing Models: Final

Logic utilization (in ALMs): 2,016 / 56,480 (4 %)

Total registers: 1781

Total pins: 41 / 268 (15 %)

Total virtual pins: 0

Total block memory bits: 0 / 7,024,640 (0 %)

Total DSP Blocks: 0 / 156 (0 %)

Total HSSI RX PCSs: 0 / 6 (0 %)

Total HSSI PMA RX Deserializers: 0 / 6 (0 %)

Total HSSI TX PCSs: 0 / 6 (0 %)

Total HSSI PMA TX Serializers: 0 / 6 (0 %)

Total PLLs: 0 / 13 (0 %)

Total DLLs: 0 / 4 (0 %)

IP Catalog

Installed IP

- Project Directory
- No Selection Available
- Library
- Basic Functions
- DSP
- Interface Protocols
- Memory Interfaces and Controllers
- Processors and Peripherals
- University Program
- Search for Partner IP

Find... Find Next

Messages

Type ID Message

- 332146 worst-case hold slack is -0.206
- 332146 worst-case recovery slack is -12.253
- 332146 worst-case removal slack is -0.076
- 332146 worst-case minimum pulse width slack is -0.317
- 332102 Design is not fully constrained for setup requirements
- 332102 Design is not fully constrained for hold requirements
- Quartus Prime Timing Analyzer was successful. 0 errors, 7 warnings
- 293000 Quartus Prime Full Compilation was successful. 0 errors, 109 warnings

System Processing (267)

100% 00:03:10

Compilation Report - FanController

Table of Contents

- Flow Summary
- Flow Settings
- Flow Non-Default Global Settings
- Flow Elapsed Time
- Flow OS Summary
- Flow Log
- Analysis & Synthesis
- Fitter
- Flow Messages
- Flow Suppressed Messages
- Assembler
- Timing Analyzer
- Summary
- Parallel Compilation
- Clocks
- Slow 1100mV 85C Model
- Fmax Summary
- Timing Closure Recommendations
- Setup Summary
- Hold Summary
- Recovery Summary
- Removal Summary
- Minimum Pulse Width Summary

Slow 1100mV 85C Model Fmax Summary

<<Filter>>

| | Fmax | Restricted Fmax | Clock Name | Note |
|---|-----------|-----------------|---------------|------|
| 1 | 17.25 MHz | 17.25 MHz | clk | |
| 2 | 72.82 MHz | 72.82 MHz | Contr...NSOR1 | |
| 3 | 96.36 MHz | 96.36 MHz | Contr...PDAT | |

This panel reports FMAX for every clock in the design, regardless of the user-specified clock periods. FMAX is only computed for paths where the source and destination registers or ports are driven by the same clock. Paths of different clocks, including generated clocks, are ignored. For paths between a clock and its inversion, FMAX is computed as if the rising and falling edges are scaled along with FMAX, such that the duty cycle (in terms of

حال برای بدست آوردن شماتیک مدار از منوی tools، Netlist Viewers، RTL-Viewer را انتخاب می‌کنیم. شماتیک برخی از قطعات مانند CU و datapath در زیر آورده شده است.

